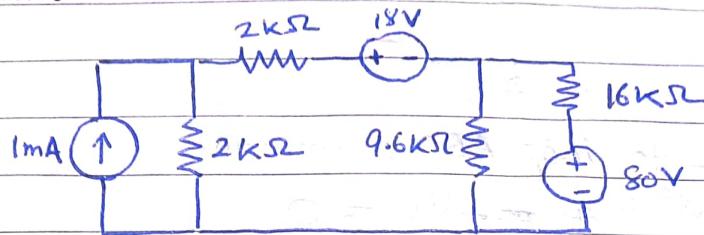


TUTORIAL - 1 - EEN - 112


HARSH PANDEY

20/19/022

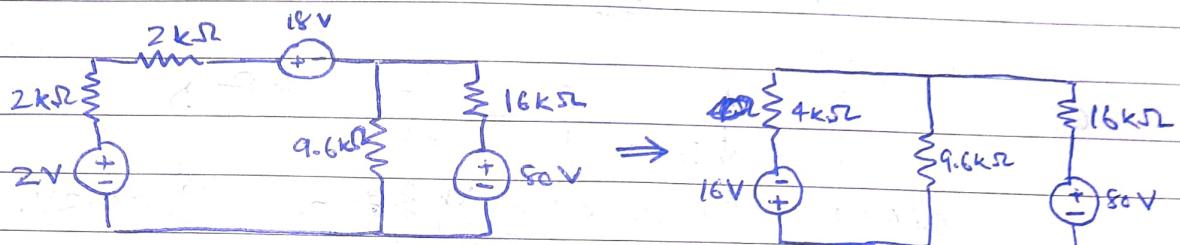
(Q1)



Transforming 1mA constant current source to a voltage source,
we have




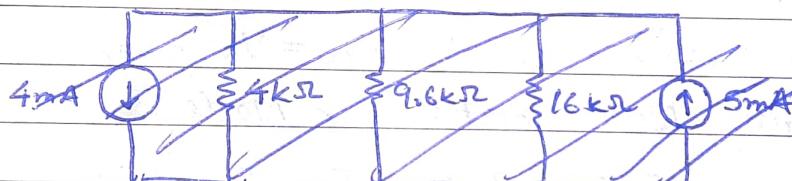Converting 16V and 80V constant voltage sources to ~~equivalent voltage sources~~, we have by Millman's theorem



$$\Rightarrow E_{eq} = \frac{E_1 + E_2}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{-\frac{16}{4} + \frac{80}{16}}{\frac{1}{4} + \frac{1}{16}} = \frac{1}{\left(\frac{5}{16}\right)} = \frac{16}{5} V$$
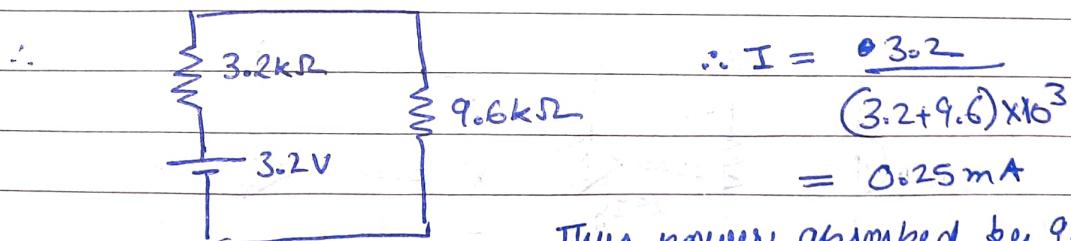
$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = \frac{16 \times 4}{20} = \frac{16}{5} k\Omega$$



$$\therefore I = 0.302$$

$$(3.2 + 9.6) \times 10^3$$


$$= 0.25 \text{ mA}$$

Thus power absorbed by 9.6kΩ resistor =

$$P = I^2 R$$

$$= (0.25 \text{ mA})^2 \times (9.6 \text{ k}\Omega)$$

$$= 0.6 \text{ mWatt}$$

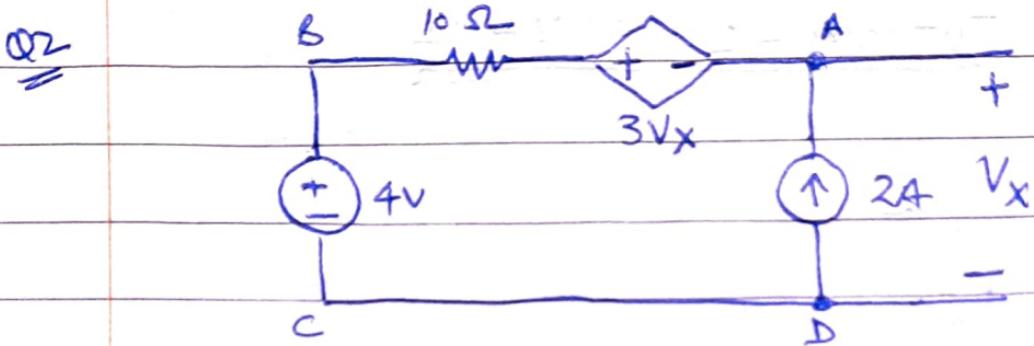


Applying KVL to loop ABCD, we have

$$+3V_x - 2(10) - 4 = +V_x = 0$$

$$\Rightarrow 4V_x = 24$$

$$\Rightarrow V_x = 6V \quad \underline{\underline{Ans}}$$

Q3

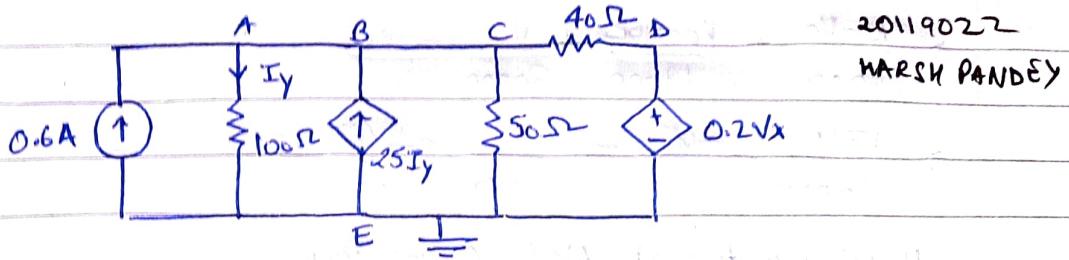

20119022

MARSH PANDEY

Let E be the reference Node at 0 Voltage

Since there is no resistance between A, B or C $\Rightarrow V_A = V_B = V_C$

Also $V_C - V_E = V_x \Rightarrow V_C = V_x$ and $V_D = 0.2V_x$.

Thus writing node equation at C, we have

$$\frac{V_C - V_D}{40} + \frac{V_C - V_E}{50} - 25I_y + \frac{V_A - V_E}{100} - 0.6 = 0$$


$$\Rightarrow \frac{V_x - 0.2V_x}{40} + \frac{V_x}{50} - 25I_y + \frac{V_x}{100} - 0.6 = 0$$

$$\text{Also } I_y = \frac{V_A - V_E}{100} = \frac{V_x}{100}$$

$$\Rightarrow \frac{0.8V_x}{40} + \frac{V_x}{50} - \frac{24V_x}{100} = 0.6$$

$$\Rightarrow -\frac{20}{100}V_x = 0.6 \Rightarrow \boxed{\underline{\underline{V_x = -3V}}}$$

Q4

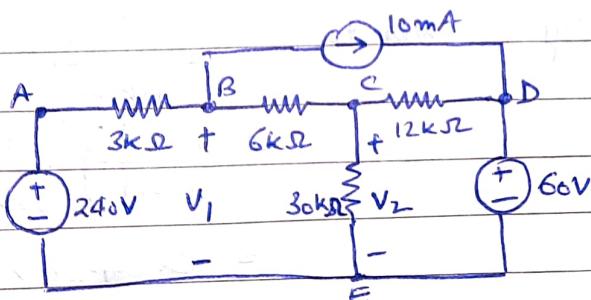

To find V_1 , V_2 and power absorbed by 6k resistor

Let E be the reference node at 0V.

$$\therefore V_A = 240V \text{ and } V_D = 60V$$

Nodal equation at Node C, we have

$$\frac{V_C - V_B}{6000} + \frac{V_C - V_D}{12000} + \frac{V_C - V_E}{30000} = 0$$

$$\Rightarrow \frac{V_C - V_B}{6000} + \frac{V_C - 60}{12000} + \frac{V_C}{30000} = 0$$

$$\Rightarrow \frac{17V_C}{60000} - \frac{V_B}{6000} = \frac{1}{200} - \textcircled{1}$$

Nodal equation at Node B, we have

$$\frac{V_B - V_C}{6000} + \frac{V_B - 240}{3000} + (10\text{mA}) = 0$$

$$\Rightarrow \frac{V_B - V_C}{6000} + \frac{V_B - 240}{3000} + 0.01 = 0$$

$$\Rightarrow \frac{V_B}{2000} - \frac{V_C}{6000} = \frac{7}{100} - \textcircled{2}$$

Multiply equation $\textcircled{2}$ by $\frac{1}{3}$ and adding to $\textcircled{1}$, we get

$$\frac{41V_C}{180000} = \frac{17}{600} \Rightarrow V_C = \frac{5100}{41} \text{V}$$


$$\Rightarrow V_B = \frac{7440}{41} \text{V}$$

$$\therefore V_2 = V_C - V_E = V_C = \frac{5100}{41} \text{V}$$


$$\therefore V_1 = V_B - V_E = V_B = \frac{7440}{41} \text{V}$$

$$\begin{aligned} \text{Power absorbed by } 6\text{k resistor} &= \frac{(V_B - V_C)^2}{6\text{k}\Omega} \\ &= \left(\frac{2340}{41}\right)^2 \frac{1}{6000} \\ &= 0.5428 \text{W} \end{aligned}$$

Q5
=

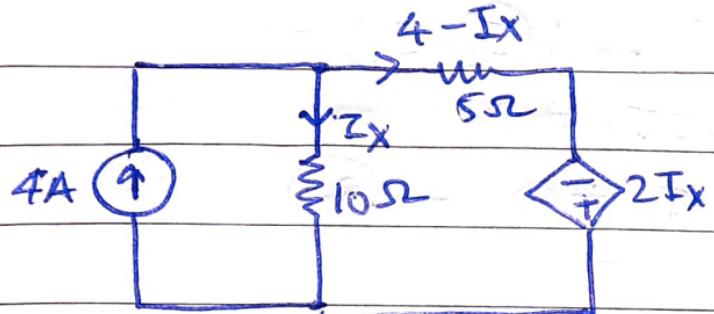



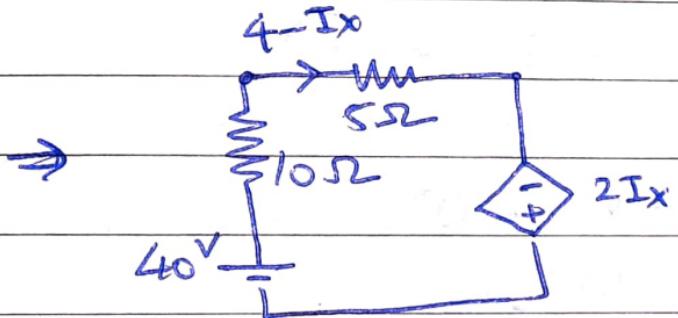
applying source transformation
on 4A independent current
source after applying current
distribution, we have



∴ In loop we have

$$\begin{aligned} & -(4 - IX)5 + 2IX + 40 - (4 - IX)10 = 0 \\ \Rightarrow & (4 - IX)15 = 40 + 2IX \\ \Rightarrow & 20 = 17IX \\ \Rightarrow & IX = \frac{20}{17} A \approx 1.1764 A \end{aligned}$$

Q6

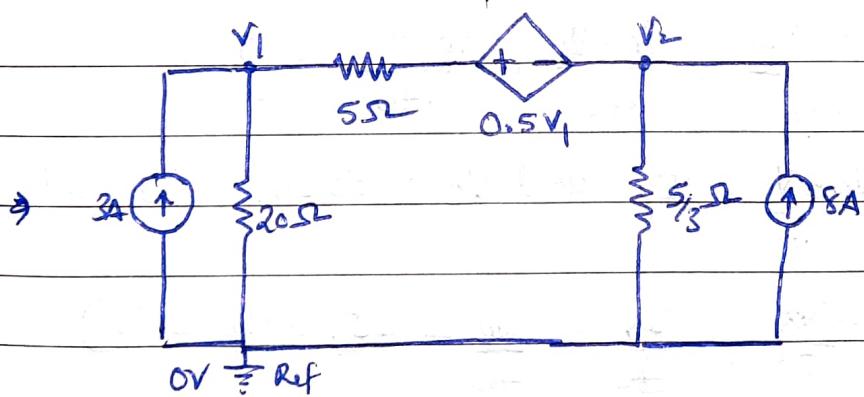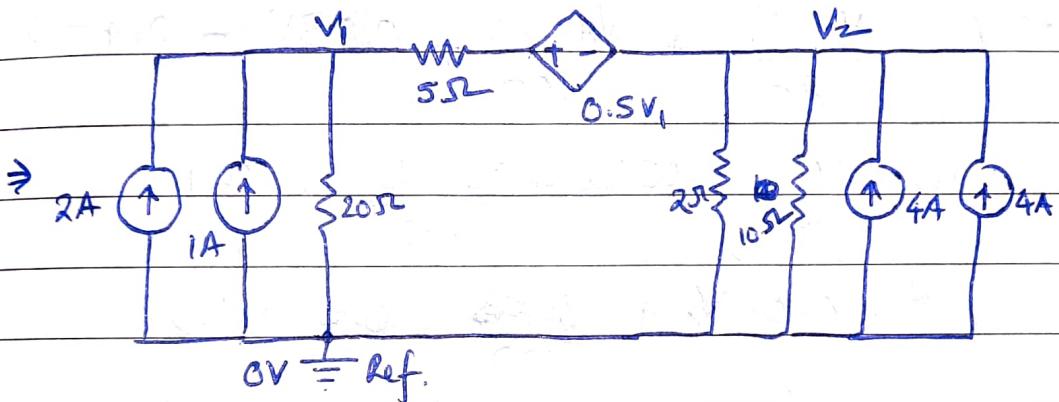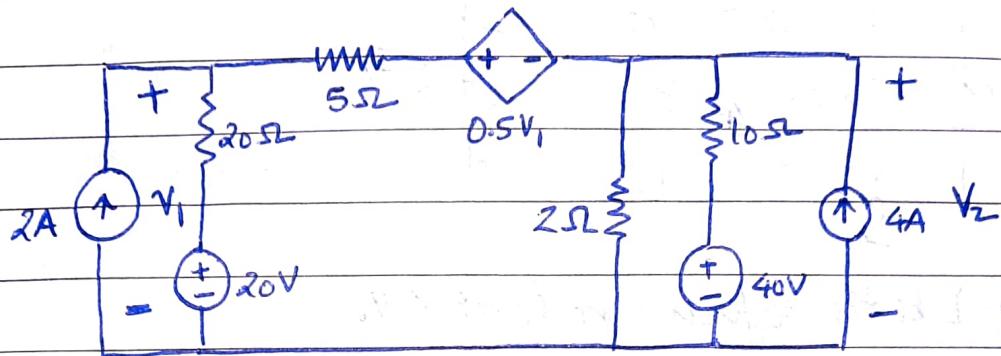

Node equation at V_1 , we have

$$\frac{V_1 - V_2 - 0.5V_1}{5} + \frac{V_1 - 0}{20} = 3 \quad \cancel{\text{---}}$$

$$\Rightarrow \frac{3V_1 - V_2}{20} = 3 \quad \text{---(1)}$$


Node equation at V_2 , we have

$$\frac{V_2 + 0.5V_1 - V_1}{5} + \frac{3V_2}{5} = 8 \Rightarrow \frac{4V_2 - V_1}{10} = 8 \quad \text{---(2)}$$

Multiplying equation ① by 4 and adding equation ②, we get

$$\frac{V_1}{2} = 20 \Rightarrow V_1 = 40V \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{ & } V_2 = 15V$$

Q7

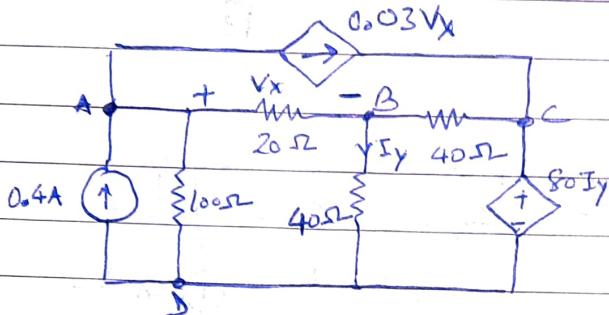

Let D be the reference node at 0V.

$$\text{At Node A: } \frac{V_A - V_B}{20} + \frac{V_A - V_D}{100} + 0.03V_x - 0.4 = 0$$

$$\Rightarrow \frac{V_x}{20} + 0.03V_x + \frac{V_A - V_D}{100} = 0.4$$

$$\Rightarrow 0.08V_x + \frac{V_A - V_D}{100} = 0.4 \quad \text{--- (1)}$$

$$\text{Node B: } \frac{V_B - V_A}{20} + \frac{V_B - V_D}{40} + \frac{V_B - V_C}{40} = 0$$

$$\text{Also } \frac{V_B - V_D}{40} = I_y \text{ and } V_C = 80I_y. \quad \{V_D = 0\}$$

$$\Rightarrow -\frac{V_x}{20} + \frac{I_y}{40} + \frac{V_B}{40} - 2I_y = 0 \quad \text{--- (2)}$$


~~$$\frac{V_x}{20} + \frac{V_B}{40} - 2I_y$$~~

$$\text{Node C: } \Rightarrow -\frac{V_x}{20} + \frac{V_B}{20} - \frac{2V_B}{40} = 0$$

$$\Rightarrow \boxed{V_x = 0}$$

$$\therefore V_A = 40V$$

Q8

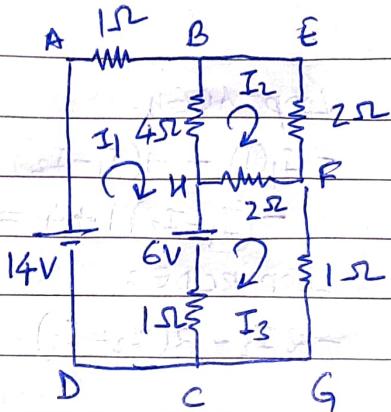

For Loop ABCD :

$$-I(I_1) - 4(I_1 - I_2) - 6$$

$$-I(I_1 - I_3) + 14 = 0$$

$$\Rightarrow 6I_1 - 4I_2 - I_3 = 8 \quad \text{--- (1)}$$

For Loop BEFH :

$$-I_2(2) - 2(I_2 - I_3) - 4(I_2 - I_1) = 0$$

$$\Rightarrow -4I_1 + 8I_2 - 2I_3 = 0$$

$$\Rightarrow -2I_1 + 4I_2 - I_3 = 0 \quad \text{--- (2)}$$

For Loop HFGC :

$$-2(I_3 - I_2) - I_3 - (I_3 - I_1) + 6 = 0$$

$$\Rightarrow -I_1 - 2I_2 + 4I_3 = 6 \quad \text{--- (3)}$$

$$6I_1 - 4I_2 - I_3 = 8 \quad \text{--- (1)}$$

$$-2I_1 + 4I_2 - I_3 = 0 \quad \text{--- (2)}$$

$$-I_1 - 2I_2 + 4I_3 = 6 \quad \text{--- (3)}$$

Subtracting (1) from (1) and adding 4x(2) to equation (3), we get

$$8I_1 - 8I_2 = 8 \quad \text{and}$$

$$-9I_1 + 14I_2 = 6$$

$$\Rightarrow -9I_1 + 14I_2 = 6 \quad \text{and} \quad I_1 - I_2 = 1$$

$$\therefore I_2 = 3A, I_1 = 4A$$

$$\Rightarrow I_3 = 4A$$

$$\begin{aligned} \text{Thus power absorbed } 4\Omega &= (I_1 - I_2)^2 R \\ &= I^2 \times 4 \\ &= 4 \text{ Watt} \end{aligned}$$

Current through 1Ω = 4A


Current through 4Ω = 1A

Current through 2Ω (b/w EF) = 3A

Current through 2Ω (b/w HF) = 1A for H to F

Current through 1Ω (b/w FG) = 4A

Current through 1Ω (b/w HC) = 0A

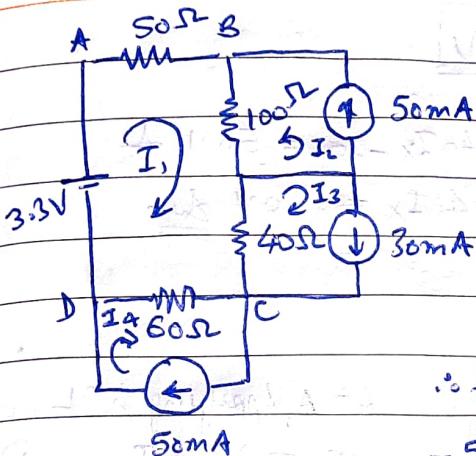

We observe that $I_2 = 50\text{mA}$, $I_3 = 30\text{mA}$ and $I_4 = 60\text{mA}$ as the corresponding loops contain independent current sources.


Let I_1 be in mA

\therefore for Loop ABCD, we have

$$\begin{aligned} -50I_1 - 100(I_1 + 50) - 40(I_1 - 30) \\ - 60(I_4 - 50) + 3300 = 0 \end{aligned}$$

$$250I_1 + 800 = 3300$$

$$\Rightarrow I_1 = 10\text{mA}$$

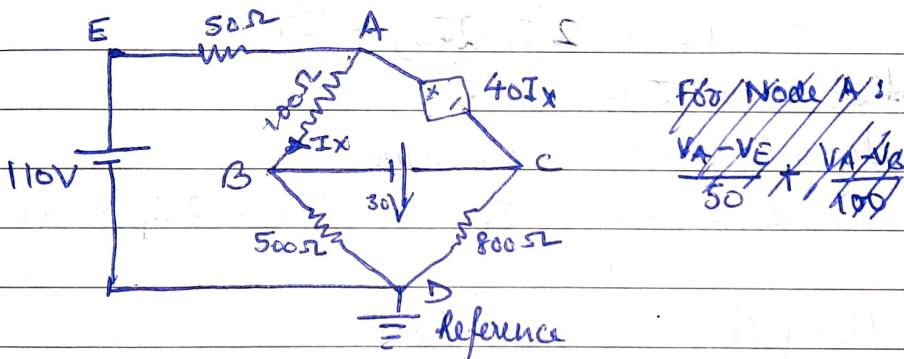

We observe $V_C = V_A - 40I_x$ and $V_B = V_C - 30$

$$\Rightarrow V_B = V_A - 40I_x - 30 \quad \text{--- (1)}$$

$$\text{Also } \frac{V_A - V_B}{100} = I_x \quad \text{--- (2)}$$

\Rightarrow Using (1) and (2), we have

$$\frac{40I_x + 30}{100} = I_x \Rightarrow I_x = 0.5A$$

At Node D, we have

$$\frac{V_D - V_B}{500} + \frac{V_D - V_C}{800} + \frac{V_D + 110 - V_A}{50} = 0$$

$$-\frac{(V_A - 40I_x - 30)}{500} + \frac{(-)(V_A - 40I_x)}{800} + \frac{110 - V_A}{50} = 0$$


$$-\frac{V_A}{500} - \frac{V_A}{800} - \frac{V_A}{50} + \frac{50}{500} + \frac{20}{800} + \frac{110}{50} = 0$$

$$\frac{93V_A}{4000} = \frac{93}{40} \Rightarrow V_A = 100 \text{ V}$$

$$\therefore V_B = V_A - 40I_x - 30 = 50 \text{ V} \quad \underline{\underline{A}}$$

$$V_C = V_A - 40I_x = 80 \text{ V} \quad \underline{\underline{B}}$$

Q11

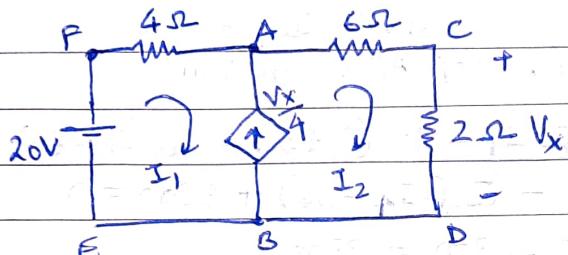

At A, applying KCL, we have
 $I_2 = \frac{V_x + I_1}{4} \quad \text{--- (1)}$

Writing loop equation for CDEF,

$$-4(I_1) - 6(I_2) - 2I_2 + 20 = 0 \quad \cancel{\text{--- (2)}}$$

$$\Rightarrow 20 = 4I_1 + 8I_2$$

$$\Rightarrow 10 = 2(I_1 + 2I_2) \quad \text{--- (2)}$$

Also $V_x = I_2(2) \quad \text{--- (3)}$

Using (1) and (3), we have

$$I_2 = \frac{2I_2}{4} + I_1 \Rightarrow I_2 = 2I_1 \quad \text{--- (4)}$$


Using (4) in (2), we have

$$10 = 2(I_1 + 2I_1)$$

$$\Rightarrow 10 = 2(5I_1)$$

$$\Rightarrow I_1 = 1 \text{ A} \quad \therefore I_2 = 2 \text{ A} \quad \underline{\underline{A}}$$

Q12

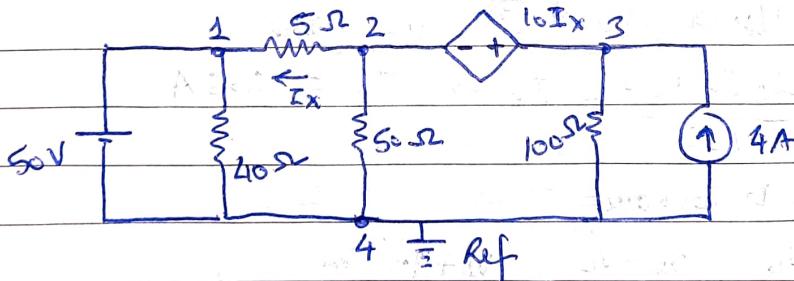

For Node 1: $V_1 = 50 \text{ V}$

For Node 2:

$$\frac{V_2 - V_1}{5} + \frac{V_2 - V_4}{50} + \frac{V_2 + 10I_x - V_4}{100} - 4 = 0$$

and $I_x = \frac{V_2 - V_1}{5}$, $V_4 = 0$

$$\Rightarrow \frac{V_2 - V_1}{5} + \frac{V_2}{50} + \frac{V_2}{100} + \frac{V_2 - V_1}{50} = 4$$


$$\Rightarrow \frac{V_2}{4} - \frac{11V_1}{50} = 4 \Rightarrow \frac{V_2}{4} - \frac{11 \times 50}{50} = 4$$

$$\therefore V_2 = 60V$$

$$\therefore I_x = \frac{V_2 - V_1}{5} = \frac{60 - 50}{5} = 2A$$

$$V_3 = V_2 + 10I_x = 60 + 10(2) = 80V$$

Q3

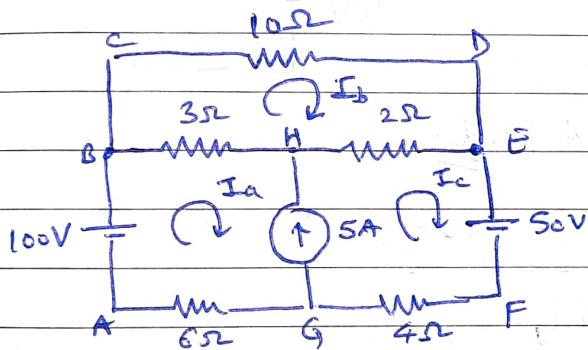

In Loop BCDE:

$$-10I_b - 2(I_b - I_c) - 3(I_b - I_a) = 0 \\ \Rightarrow 15I_b - 3I_a - 2I_c = 0 \quad \text{--- (1)}$$

In Loop BEFA:

$$-3(I_a - I_b) - 2(I_c - I_b) - 50 \\ - 4I_c - 6I_a + 100 = 0$$

$$\Rightarrow 9I_a - 5I_b + 6I_c = 50 \quad \text{--- (2)}$$

Also Applying KCL at 'H', we have $I_a + 5 = I_c$ ~~+ 5~~ $\Rightarrow I_a + 5 = I_c$ $\quad \text{--- (3)}$


$$15I_b - 3I_a = 2I_B + 2I_a + 10 \Rightarrow 15I_b - 5I_a = 10$$

$$9I_a - 5I_b + 6I_a + 30 = 50 \Rightarrow 15I_a - 5I_b = 20$$

$$I_b = \frac{5}{4}A = 1.25A$$

$$\therefore I_a = \frac{7}{4}A = 1.75A$$

$$\text{Now } I_c = I_a + 5 = 6.75A$$

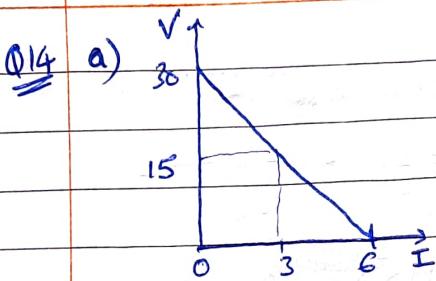

From graph, equation of straight line
is, $V = 30 - 5I$

\therefore A voltage drop of $30V$ can be produced regardless of current \rightarrow source present of $30V$, which is independent in nature.


\therefore A voltage drop occurs linearly in direction of ~~the~~ current hence a resistance ~~of~~ (ideal) is present.

$$R = |\text{slope}| = 5\Omega$$

b) Applying KVL

$$30 - 5I - 10I = 0$$


$$\Rightarrow I = 2A$$

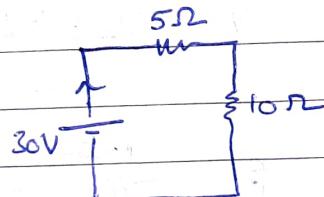

$$\text{Power} = I^2R = 2^2(10)$$

$$= 40W \underline{\underline{}}$$

Q15

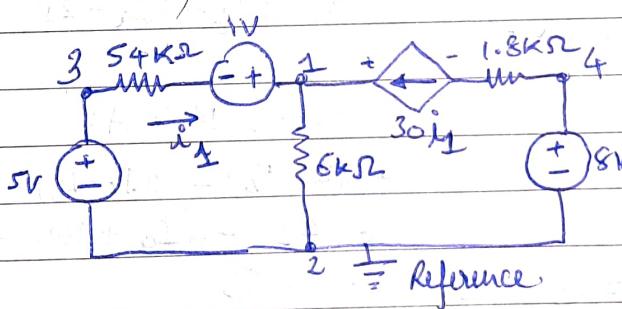

$$i_2 = \frac{-V_1 + 1 + V_3}{54000}$$


For Node 1; we have

$$\frac{V_1 - V_2}{6000} = 30i_1 + \frac{V_1 - 1 - V_3}{54000} = 0$$

$$\frac{V_1}{6000} = \frac{39}{54000} \left(\frac{6 - V_1}{54000} \right) = 0$$

$$\Rightarrow \frac{39 \times 6}{54000} = \frac{40V_1}{54000} \Rightarrow V_1 = 4.65V \underline{\underline{}}$$
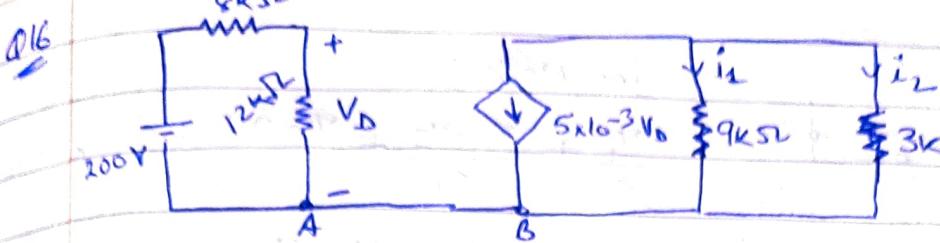
$$\therefore I_1 = \frac{6 - 4.65}{54000} = 25\mu A \underline{\underline{}}$$




$$V_D = \frac{12 \times 10^3 (200)}{(8+12) \times 10^3} = 120\text{ V} \quad (\text{branch AB has no current})$$

as $V_A = V_B$

$$\therefore \text{Current by dependent current source} = 5 \times 10^{-3} \times V_D \\ = 5 \times 10^{-3} \times 120 \\ = 0.6\text{ A}$$

$$\therefore \text{Current in } 9\text{ k}\Omega = 0.6 \times \frac{3}{9+3} = 0.15\text{ A} \Rightarrow \text{in } 3\text{ k}\Omega = 0.45\text{ A}$$
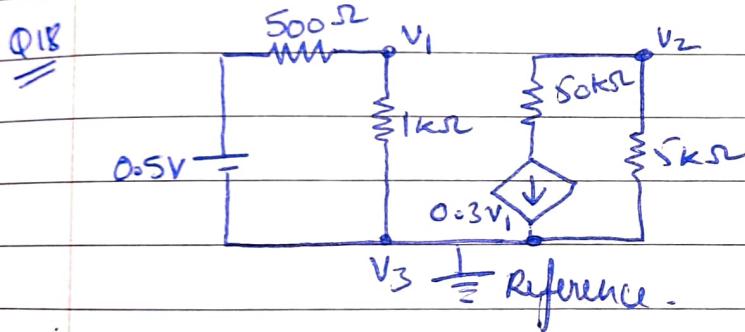
$$\Rightarrow i_1 = -0.15\text{ A} \quad \text{and} \quad i_2 = -0.45\text{ A}$$



For Node V₁:

$$\frac{V_1 - V_3}{1000} + \frac{V_1 - 0.5}{500} = 0$$

$$\Rightarrow \frac{3V_1}{1000} = \frac{0.5}{500} \Rightarrow V_1 = \frac{1}{3}\text{ V}$$


$$\therefore \text{Current supplied by dependent source} = 0.3V_1 = 0.1\text{ A}$$

\therefore Power supplied by 0.5 V source =

$$I = \frac{0.5}{1500} = \frac{1}{3}\text{ mA}$$

$$\therefore P = VI = 0.5 \times \frac{1}{3} \times 10^{-3} = \frac{1}{6}\text{ mW} \underline{\underline{}}$$

Q19

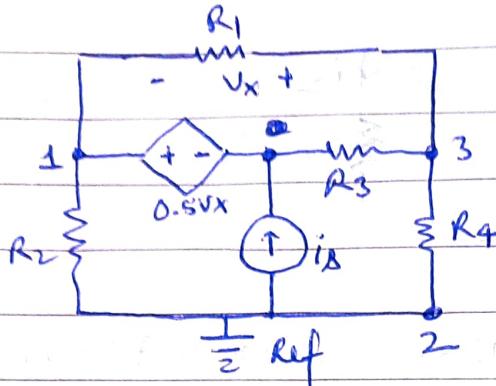

for Node 1:

$$\frac{V_1}{R_2} + \frac{V_1 - V_3}{R_1} + \frac{V_1 - 0.5Vx - V_3}{R_3} = i_B$$

$$\Rightarrow \frac{V_1}{R_2} + \frac{V_1 - V_3}{R_1} + \frac{V_2 - V_3}{R_3} = I_B - \textcircled{1}$$

for Node 2

~~$$I_B = \frac{V_2 - V_3}{R_3} + \frac{V_1 - V_3}{R_1} + \frac{V_1}{R_2}$$~~

$$\text{for Node 2 : } I_S = \frac{V_3}{R_4} + \frac{V_1}{R_2} - \textcircled{2}$$

$$\text{for Node 3 : } \frac{V_3}{R_4} + \frac{V_3 - V_2}{R_3} + \frac{V_3 - V_1}{R_1} = 0 - \textcircled{3}$$